

28V 1A Boost Converter

3.3V Input

28V 1A Output

200kHz switching frequency

LT3757 IC

Niyazi Emirhan Yeşil

28V 1A Boost Converter

Design Steps

1. System parameters and design constraints
2. Examination of working mods of System and Power IC
3. Duty cycle calculation (Duty)
4. Inductor selection (L)
5. Output capacitor selection (C)
6. Diode selection(D)
7. Switching component selection(Q)
8. Configuration of power IC's peripherals (UVLO, RT etc.)

28V 1A Boost Converter

Tasarım Adımları

9. Input capacitor selection
10. Defining control Loop parameters
11. Spice Simulation ve design validation
12. Schematic design
13. PCB Layout design

28V 1A Boost Converter

1. System parameters and design constraints

1. Input Voltage (V_{in}) = 3.3V
2. Output Voltage (V_{out}) = 28V
3. Output Current (I_{out}) = 1.0A
4. Output Power (P_{out}) = 28W
5. Switching frequency (f_{sw}) = 200kHz
6. %d V_o /dt: 0.1%
7. %d I_L /dt: 25%



28V 1A Boost Converter

2. Examination of working mods of System and Power IC


1. Input Voltage (V_{in}) = 3.3V
2. Output Voltage (V_{out}) = 28V
3. Output Current (I_{out}) = 1.0A
4. Output Power (P_{out}) = 28W
5. Switching frequency (f_{sw}) = 200kHz
6. %d V_o /dt: 0.1%
7. %d I_L /dt: 25%



LT3757

Boost Controller IC

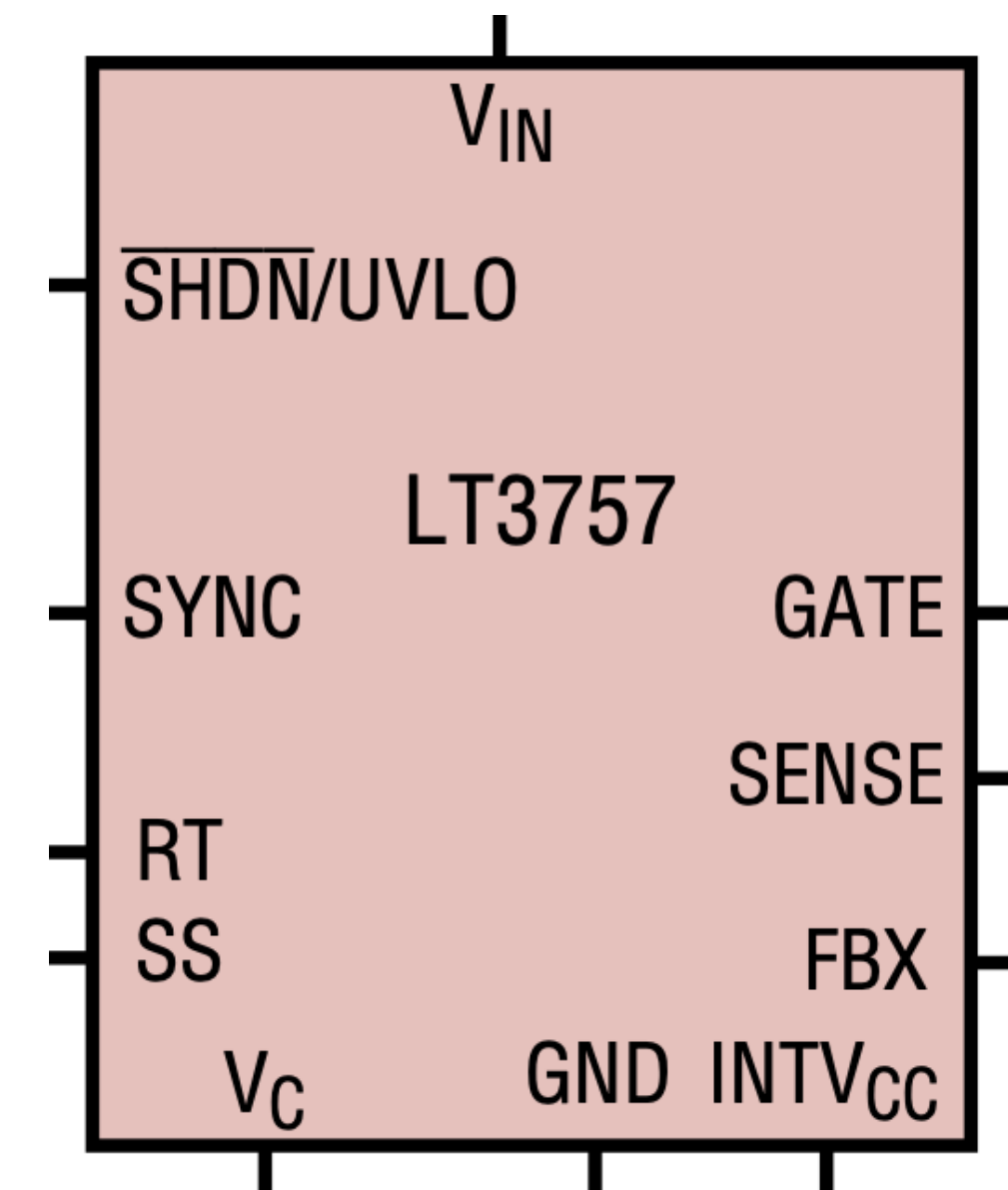- V_{in} range: 2.9V to 40V
- Operating frequency: 100kHz-1MHz
- Current mode control
- Synchronizable to External Clock
- UVLO feature at 1.22V with Hysteresis
- Soft start, Frequency foldback



28V 1A Boost Converter

3. Duty cycle value calculation (ideal Duty)

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 - D} \text{ (ideal boost converter)}$$

$$D = \frac{V_{out} - V_{in}}{V_{in}} = \frac{28 - 3.3}{28} = 0.882 \quad \%88.2 \text{ Duty cycle (Ideal duty cycle)}$$

28V 1A Boost Converter

4. Inductor selection (L)

Average Inductor Current

$$I_L = \frac{V_{in}}{R * (1 - D)^2} = \frac{3.3}{28 * (1 - 0.8821)^2} = 8.484A$$

$$\Delta I_L = \% \Delta I_L * I_L = 0.25 * 8.484A = 2.121A$$

$$I_{L_{peak}} = I_L + \Delta I_L = 8.484 + 2.121 = 10.606A$$

$$I_{L_{sat}} = I_{L_{peak}} * S = 10.606 * 1.5 = 15.909A$$

$$\Delta I_L = \frac{V_{in} D T_{sw}}{2L}$$

$$L \geq \frac{V_{in} D}{2 \Delta I_L f_{sw}}$$

$$L \geq \frac{3.3}{2 * 2.121 * 200000}$$

$$L \geq 3.431 \mu H \quad \text{closest commercial inductor value } 3.9 \mu H$$

28V 1A Boost Converter


4. Inductor selection (L)

$R_L \leq 0.0975\text{ohm}$ boundary condition

The graph in the right side of the page, numerically obtained value of the inductor internal resistance must be equal or less than 0.0975ohm, if not the desired V_{out}/V_{in} ration will not be achieved.

A small R_L will reduce the duty cycle value and have a positive contribution to efficiency.

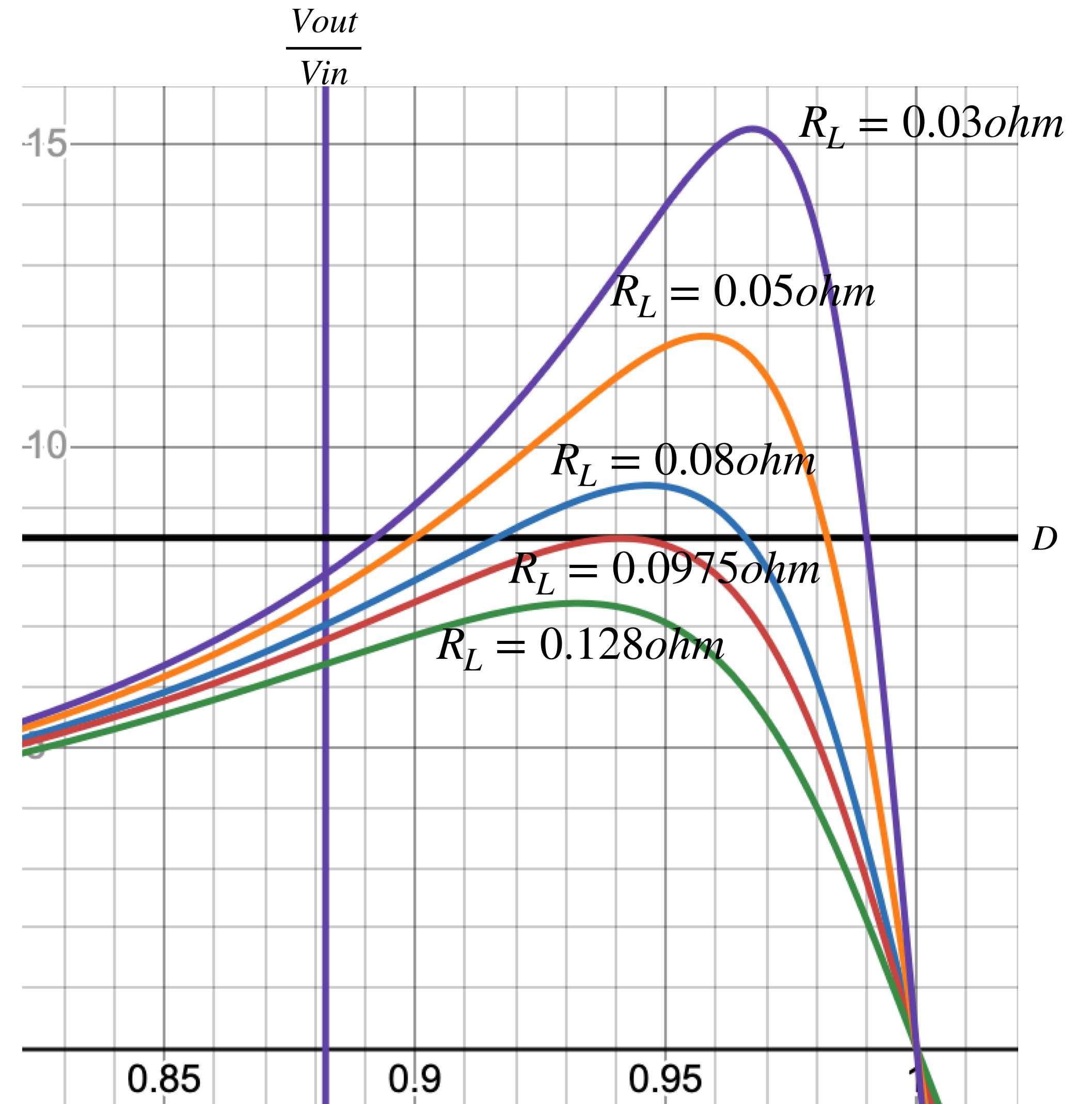By this reason R_L value will be selected equal or less than $R_L \leq 0.01\text{ohm}$.



28V 1A Boost Converter

4. Inductor selection (L)

The coil that best meets these criteria was selected as the coil with the product number 7443556450 from Würth Elektronik.


$$L = 4.5\mu\text{H}$$

$$I_L \text{ rated} = 20.5\text{A}$$

$$I_{\text{sat}} = 37\text{A}$$

$$\text{DCR}_{\text{max}} = 3.4\text{mohm}$$

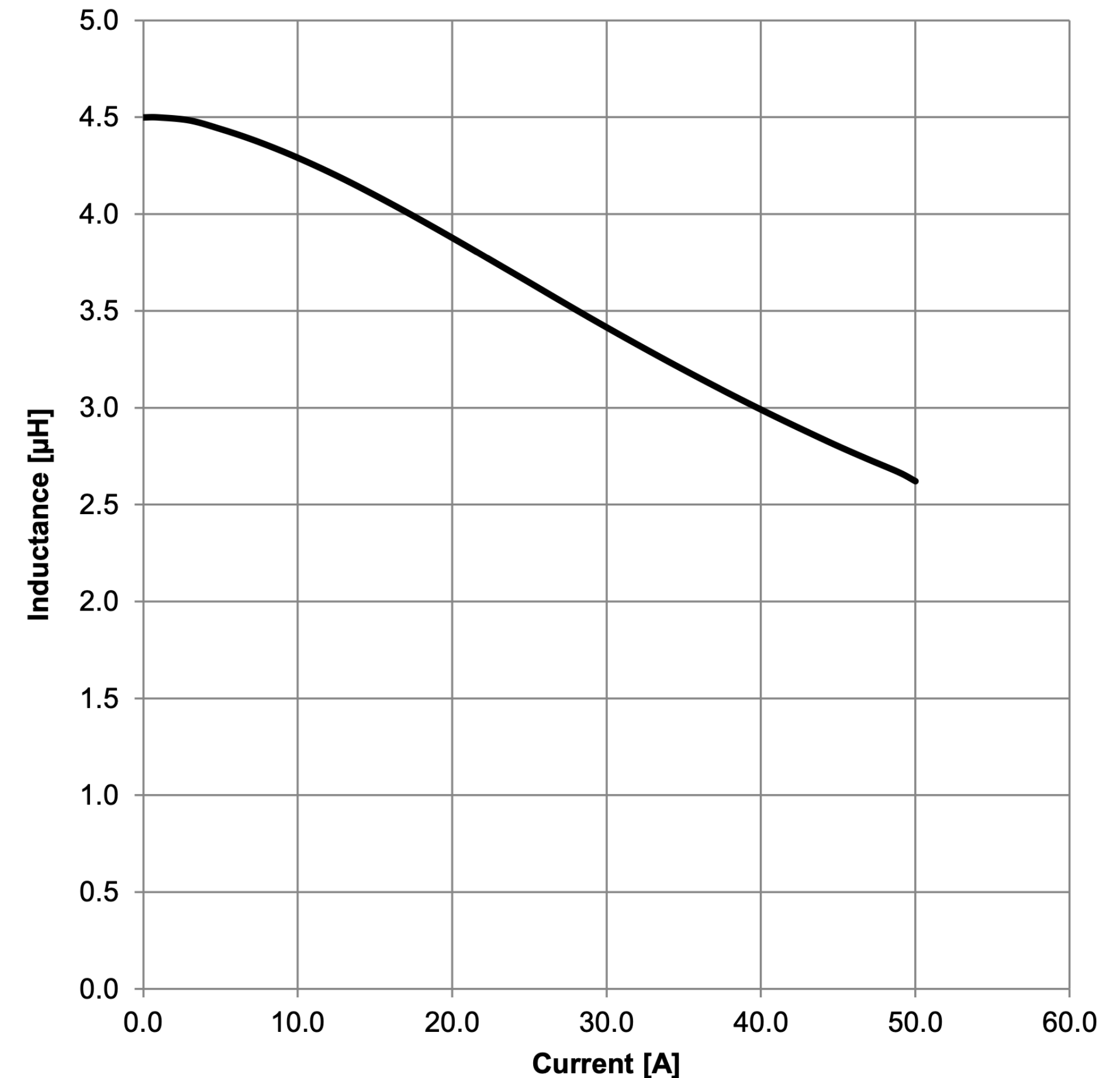Typical Inductance vs. Current Characteristics:



28V 1A Boost Converter

5. Output Capacitor Selection (Cout)

$$\Delta V_{out} = \frac{V_{out} * D}{2 * R * C_{out} * f_{sw}}$$

$$\Delta V_{out} = \% \Delta V_{out} * V_{out} = 0.001 * 28 = 0.028 = 28mV$$

$$C_{out} = \frac{V_{out} * D}{2 * R * \Delta V_{out} * f_{sw}} = \frac{28 * 0.848}{2 * 28 * 0.028 * 200000} \geq 78.76\mu F$$

$$C_{out} = 100\mu F \text{ seçildi}$$

$$ESR \leq \frac{\Delta V_{out}}{\frac{I_{outmax}}{1-D} + \Delta I_L} = \frac{0.028}{\frac{1.001}{1-0.882} + 2.121} \leq 2.63mohm$$

28V 1A Boost Converter

5. Output Capacitor Selection (C_{out})

In order to reduce the ESR in the output capacitor, two 39 μ F 50SVPF39M electrolytic capacitors and two C1210C106K5RAC7800 MLCC capacitors will be used.

28V 1A Boost Converter

6. Diode selection (D)


$$I_{D_{peak}} = I_{L_{peak}} = 10.606A$$

$$I_{D_{max}} = I_D * 1.5 = 15.909A$$

$$V_{D_{VRRM}} \sim V_{out} = 28V$$

$$V_{D_{VRRM}max} = 28 * 1.5 = 42$$

$$V_{D_{VRRM}max} \geq 42V$$

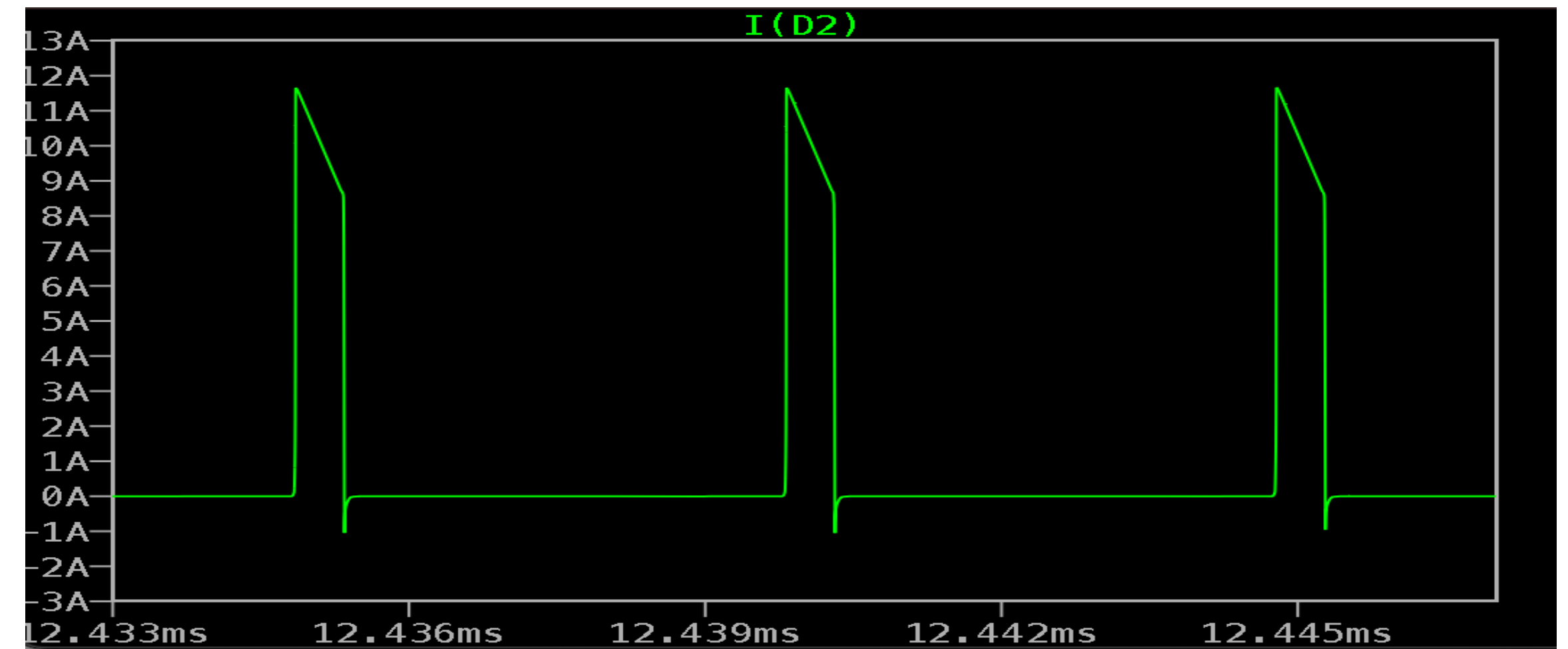

28V 1A Boost Converter

6. Ploss of Diode

1. Forward power loss (Pf)

As a result of the calculations made

The diode RBQ30NS45B from Rohm company was selected.

$$P_f = V_f * I_d = 0.590W$$



RBQ30NS45B

28V 1A Boost Converter

7. Switching component selection(Q)

$$V_{ds} = V_{out} + V_f = 28 + 0.5V = 28.5V$$

The maximum Vds is multiplied by the 1.5 safety factor, and the minimum Vds value that the switching element must have is 42.75V. For this reason, a switching element with a minimum Vds value of 50V has been selected.

$$I_{mosfet_{peak}} = I_{L_{peak}} = 10.606A$$

$V_{gs_{th}} \leq 3V$ The maximum voltage that the gate driver of the LT3757 integrated circuit can provide is 3.3V.

$$P_{fet} = I_L^2 * r_{dson} * D + 2 * V_{out}^2 * I_{L_{peak}} * C_{RSS} * f_{sw} / 1 = 1.8W$$

Infineon IPD079N06L3 mosfet was selected as a mosfet suitable for these conditions.

28V 1A Boost Converter

8. Configuration of power IC's peripherals (UVLO, RT etc.)

1. Rsense resistor selection

$$R_{sense} = \frac{80mV}{I_{Lpeak}} = 6.8m\Omega$$

$$P_{Rsense} = \frac{80mV^2}{R_{sense}} = 933mW$$

$$\Delta V_{sense} = \Delta I_{Lpeak} * R_{sense} = 30mV$$

$$X = \frac{\Delta V_{sense}}{80mV - 0.5 * \Delta V_{sense}} = 0.44$$

The Vishay Dale WSL25126L800FEA18 6.8mR 2W resistor was selected to meet these conditions.

28V 1A Boost Converter

8. Configuration of power IC's peripherals (UVLO, RT etc.)

2. Voltage feedback resistor selection


For $R_{top} = 33k$;

$$R_{bot} = R_{top} * \frac{V_{fb}}{V_{out} - V_{fb}} = 2k\Omega$$

0.1% precision resistors were used as tolerance.

R_{top} 33k: ERA-3AEB333V

R_{bot} 2k: ERA-3AEB202V

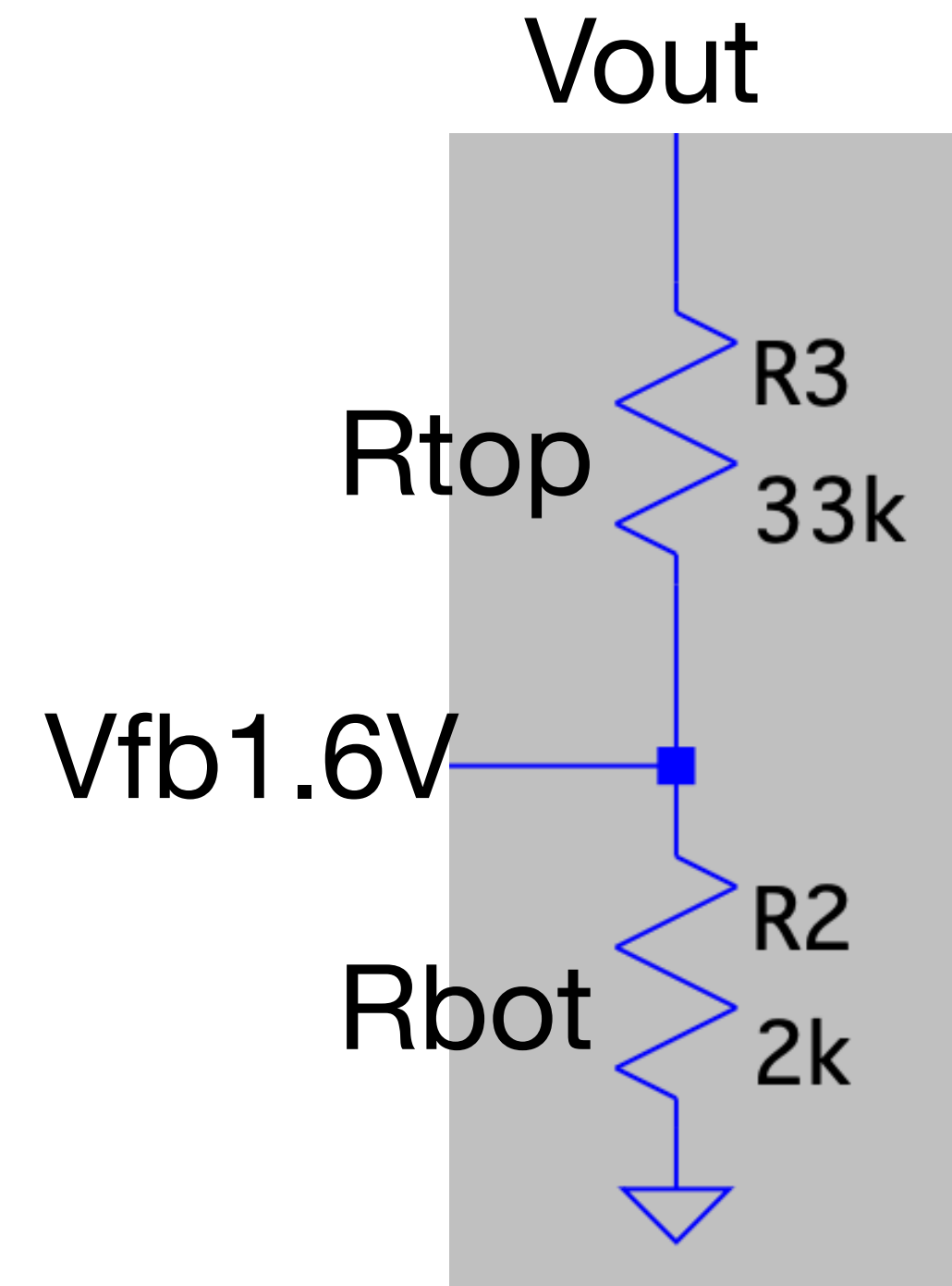

28V 1A Boost Converter

8. Configuration of power IC's peripherals (UVLO, RT etc.)

3. Under Voltage Lock Out resistor selection

V_{uvlo} voltage is chosen 2.4V


For R_{top} = 33k

$$R_{bot} = R_{top} * \frac{V_{uvlo}}{V_{in} - V_{uvlo}} = 33k\Omega$$

0.1% tolerance precision resistors were used.

R_{top} 33k: ERA-3AEB333V

R_{bot} 33k: ERA-3AEB333V

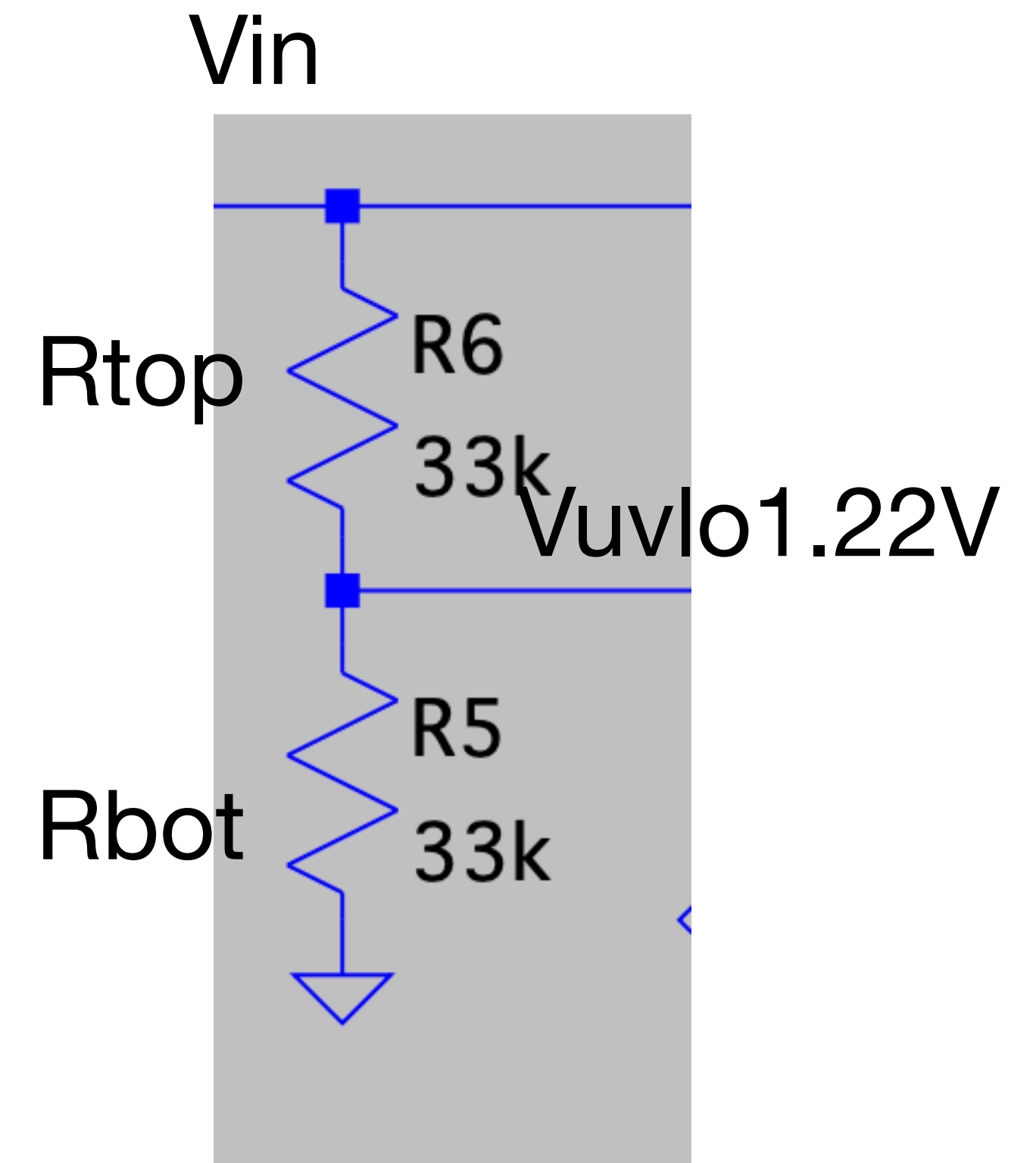


28V 1A Boost Converter

8. Configuration of power IC's peripherals (UVLO, RT etc.)

4. Rt resistor selection

The Rt resistance value is obtained from the graph on the side taken from the datasheet. According to this graph, a resistor of 68k will allow the IC to operate at a frequency of 200kHz.

Rt = 68k : ERA-6AEB683V

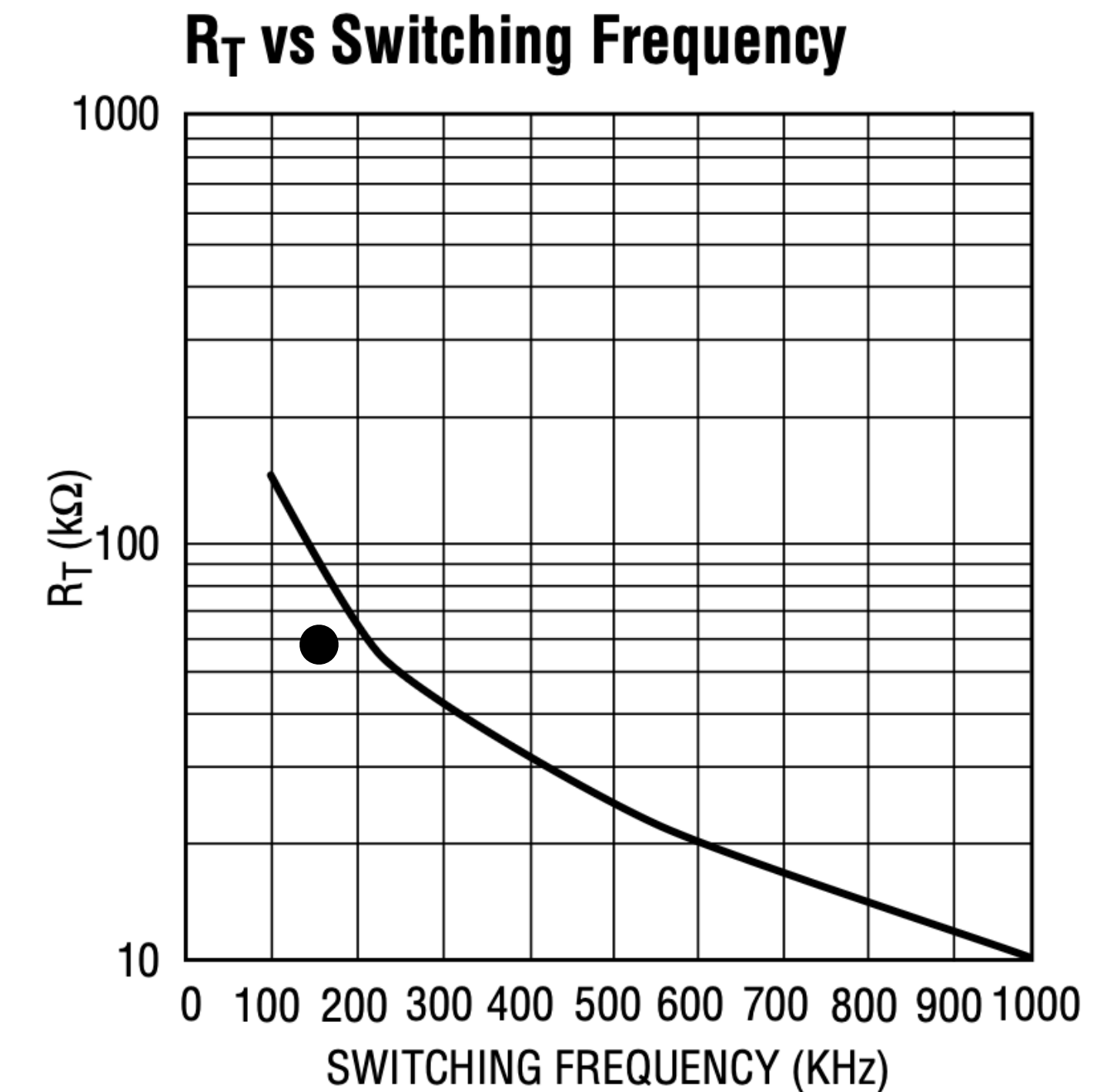

28V 1A Boost Converter

8. Configuration of power IC's peripherals (UVLO, RT etc.)

5. Soft Start (SS) capacitor

To ensure that the system performs an 8ms soft start

$$C_{ss} = T_{ss} * \frac{10\mu A}{1.25V} = 64nF \text{ approximately } 68nF$$

C_{ss} = 68nF : C0603C683J1RACTU %5 tolerance was chosen

28V 1A Boost Converter

8. Configuration of power IC's peripherals (UVLO, RT etc.)

6. INTVcc capacitor selection

A capacitor of 4.7uF value specified in the datasheet was preferred. The voltage was selected as 35V.

$C_{intVcc} = 4.7\mu F$: GRM188R6YA475KE15D was chosen.

28V 1A Boost Converter

9. Input Capacitor Selection

The input capacitor must have a very low ESR value.


For this design $<6\text{mohm}$.

For this reason, three parallel 56uF EEH-ZV1J560P capacitors were selected.

28V 1A Boost Converter

11. Spice Simulation and Design Validation



1. Spice simulation schematic

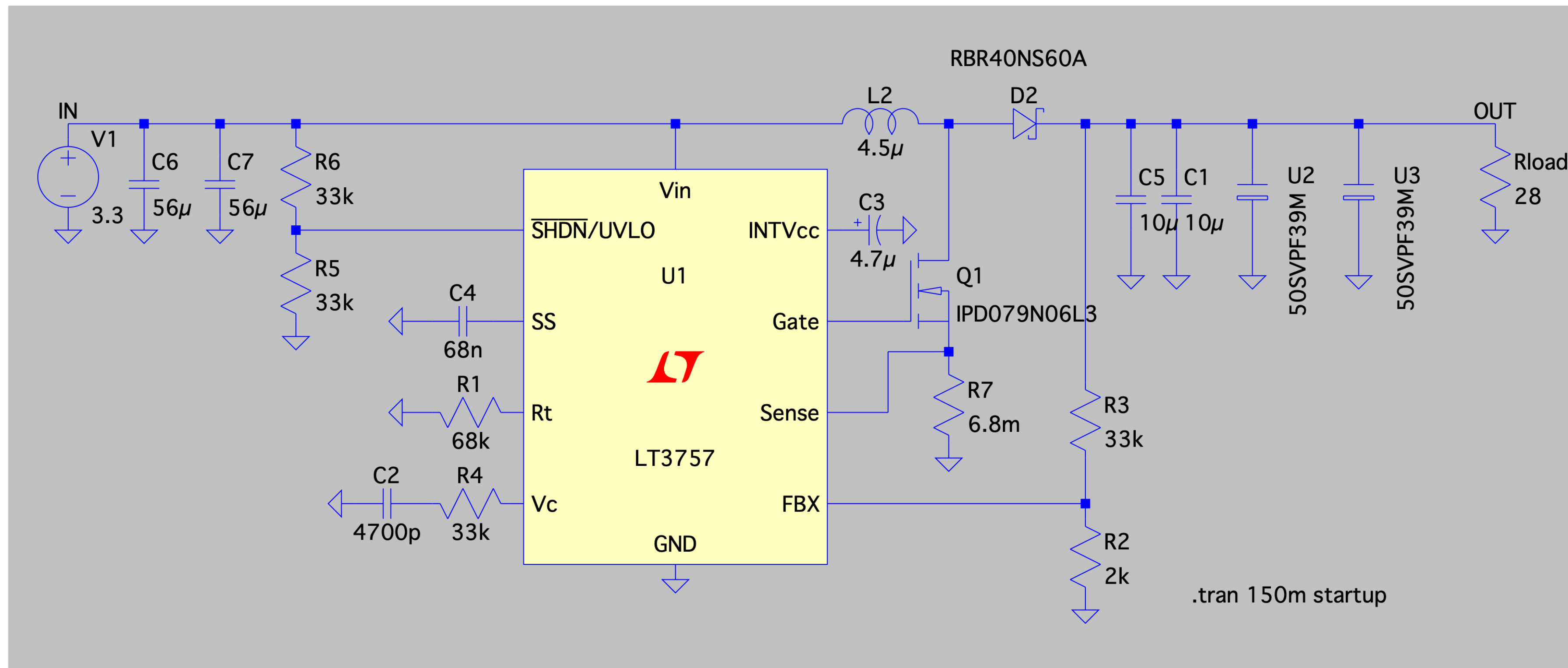

28V 1A Boost Converter


11. Spice Simulation and Design Validation

1. Output Voltage simulation

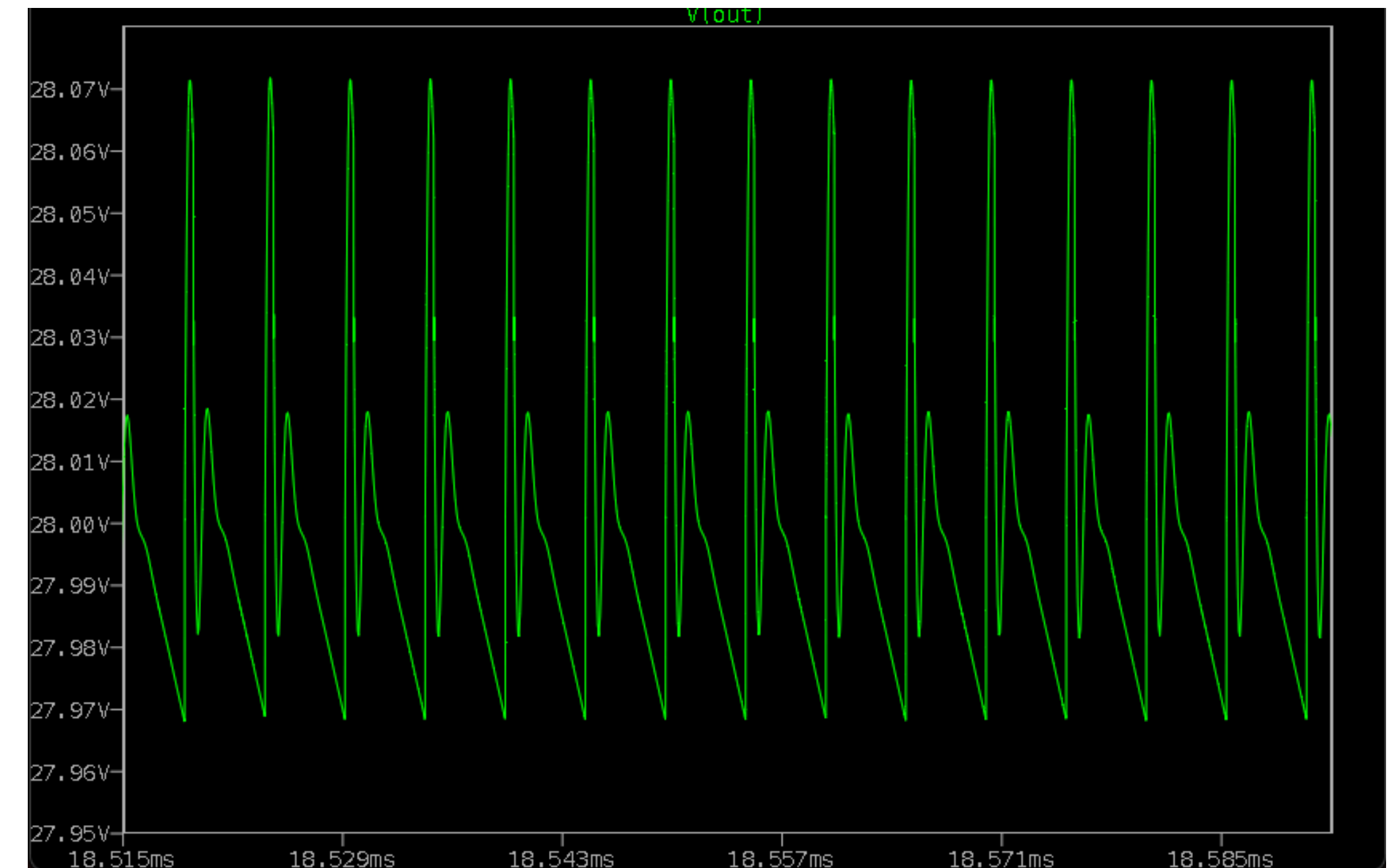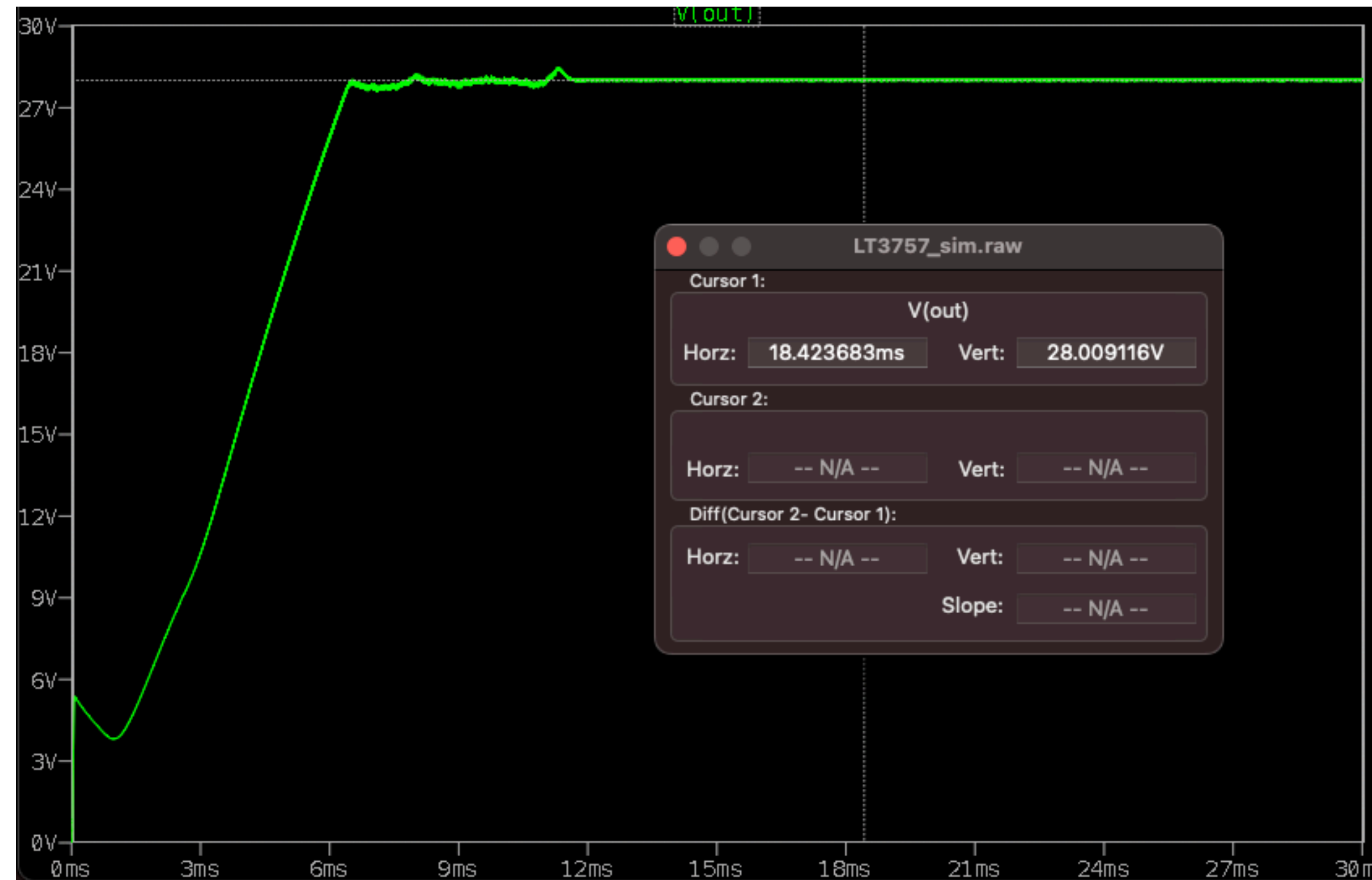


28V 1A Boost Converter

12. Schematic Design

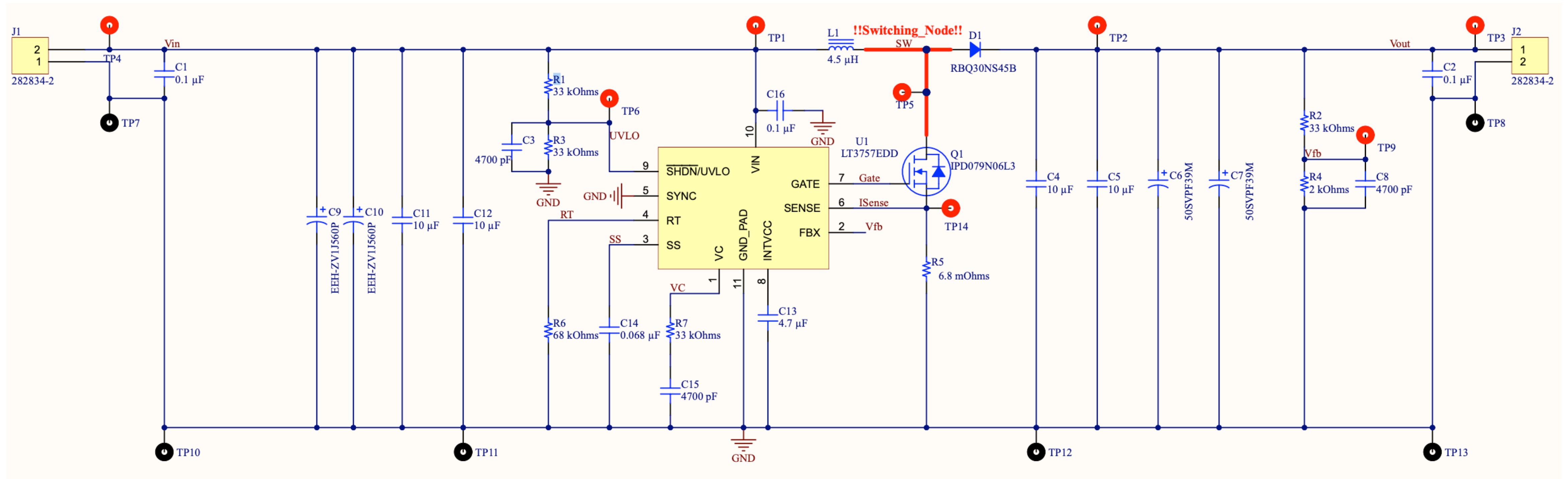

28V 1A Boost Converter


13. PCB Layout Design

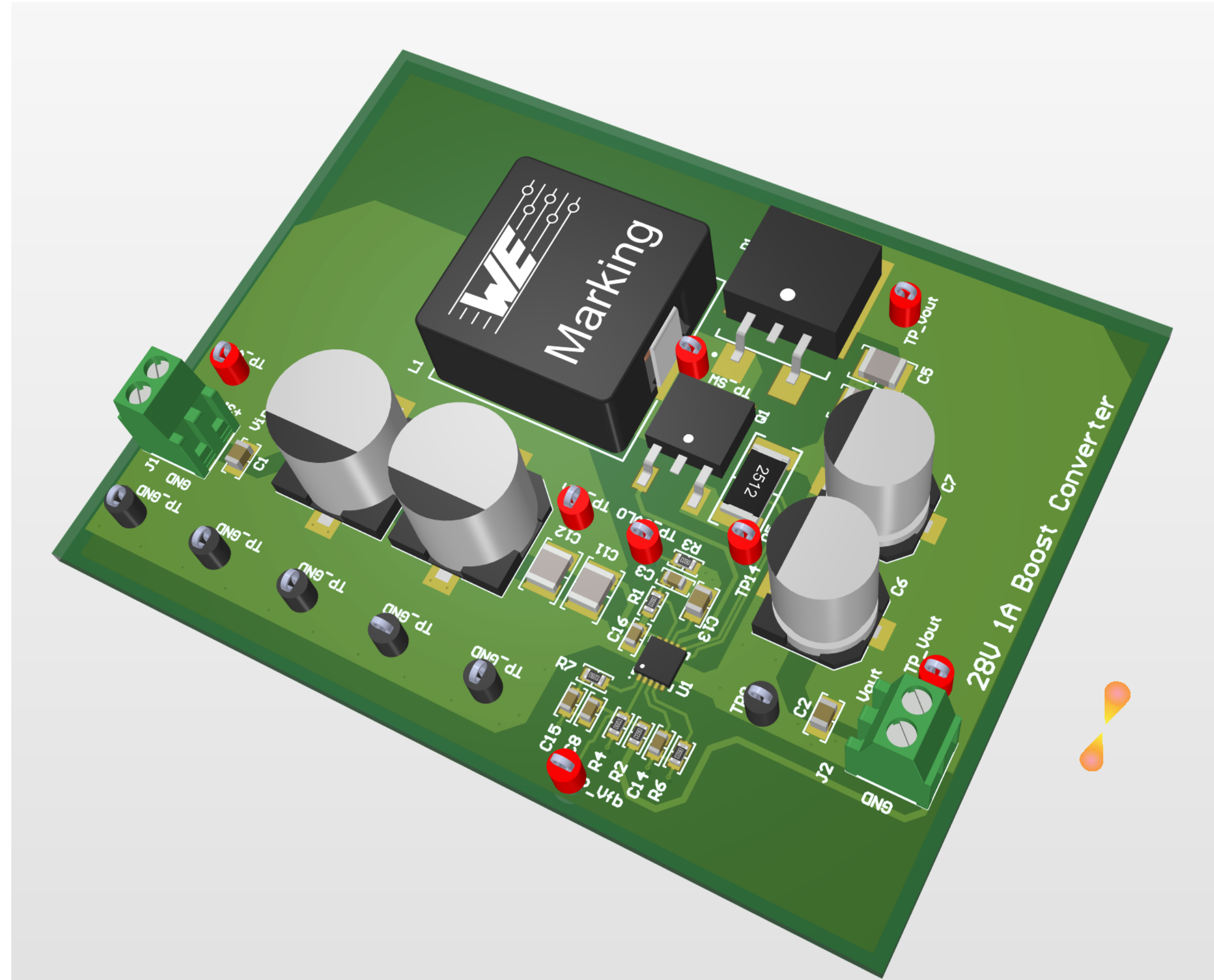

3D Görünüm

28V 1A Boost Converter


13. PCB Layout Design

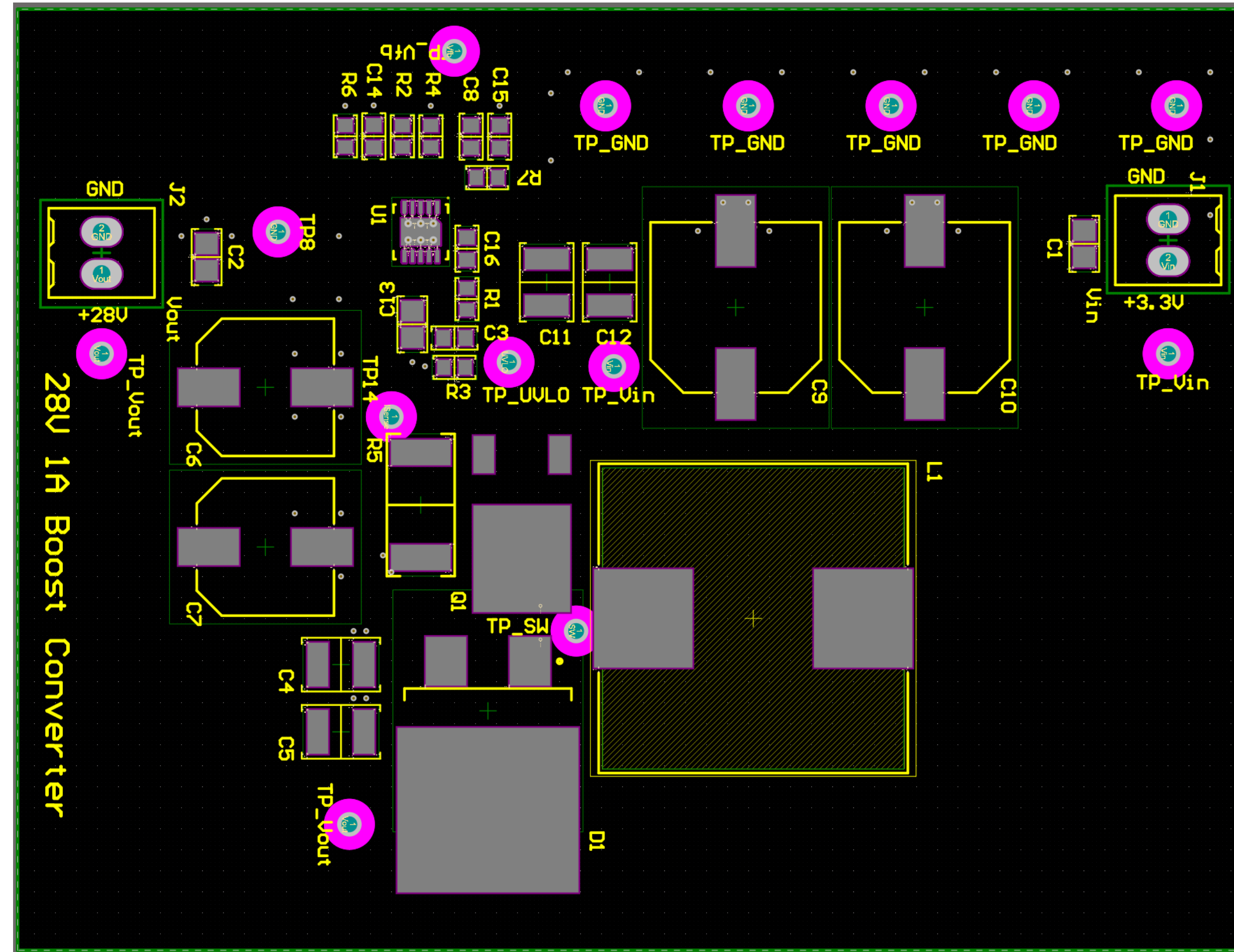

Komponent Yerleşimi

28V 1A Boost Converter

13. PCB Layout Design

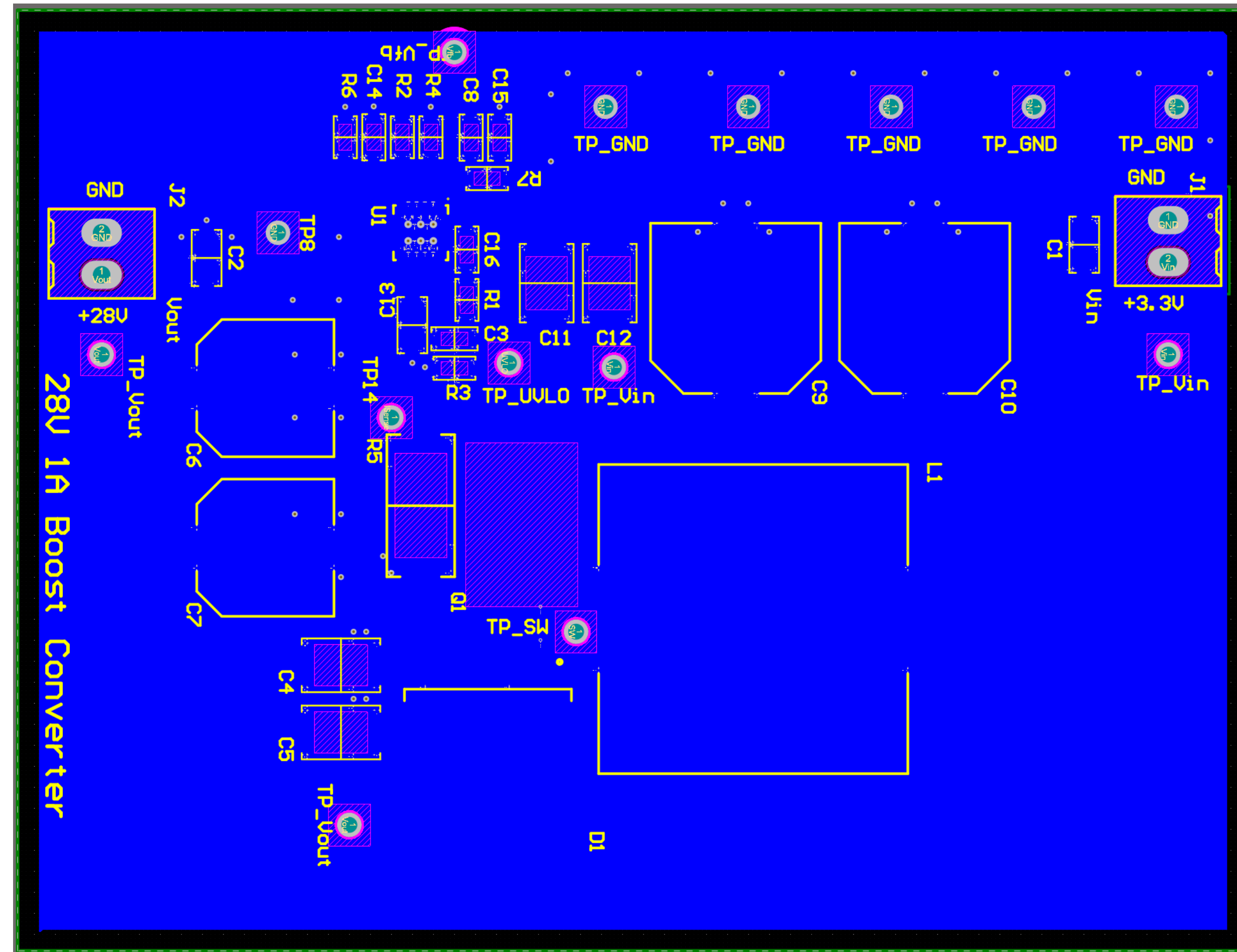

Bottom Layer